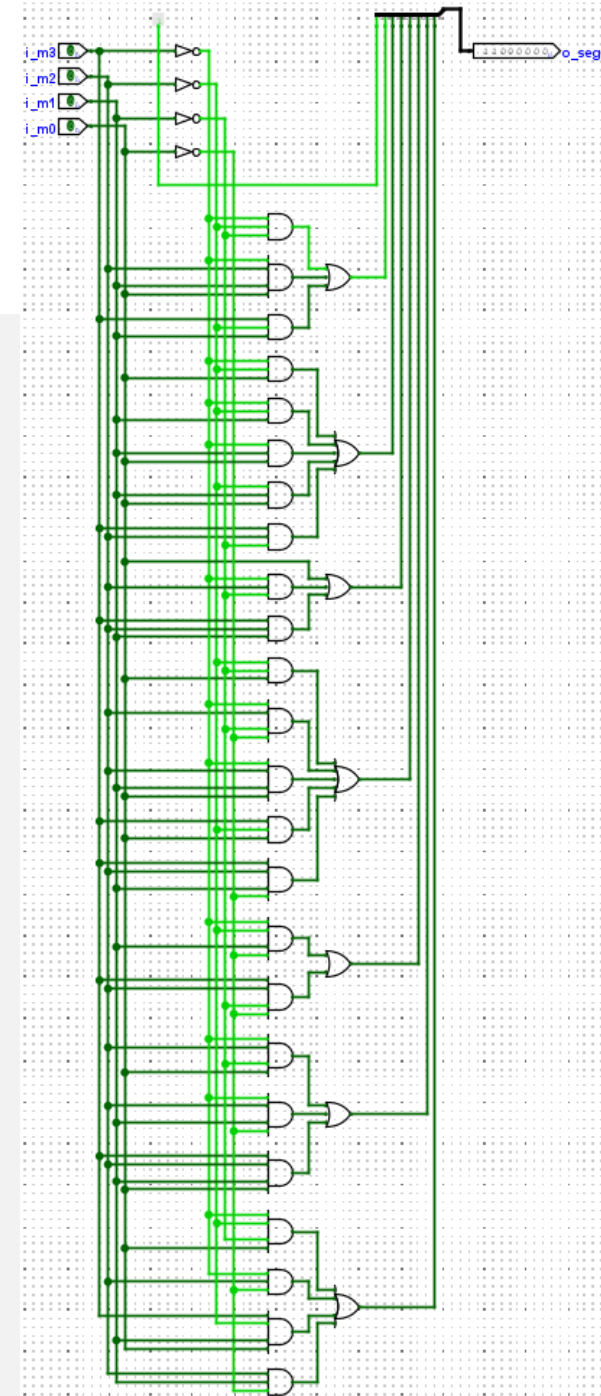


Lab 4 Marshall Harrell

7seg decoder


i_m3	i_m2	i_m1	i_m0	o_seg[7..0]
0	0	0	0	1 1 0 0 0 0 0 0
0	0	0	1	1 1 1 1 1 0 0 1
0	0	1	0	1 0 1 0 0 1 0 0
0	0	1	1	1 0 1 1 0 0 0 0
0	1	0	0	1 0 0 1 1 0 0 1
0	1	0	1	1 0 0 1 0 0 1 0
0	1	1	0	1 0 0 0 0 0 1 1
0	1	1	1	1 1 1 1 1 0 0 0
1	0	0	0	1 0 0 0 0 0 0 0
1	0	0	1	1 0 0 1 1 0 0 0
1	0	1	0	1 1 0 0 0 0 0 0
1	0	1	1	1 1 1 1 1 0 0 1
1	1	0	0	1 0 1 0 0 1 0 0
1	1	0	1	1 0 1 1 0 0 0 0
1	1	1	0	1 0 0 1 1 0 0 1
1	1	1	1	1 0 0 1 0 0 1 0




Circuit B

2 of 2 rows shown

z	s6	s5	s4	s3	s2	s1	s0
0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	1

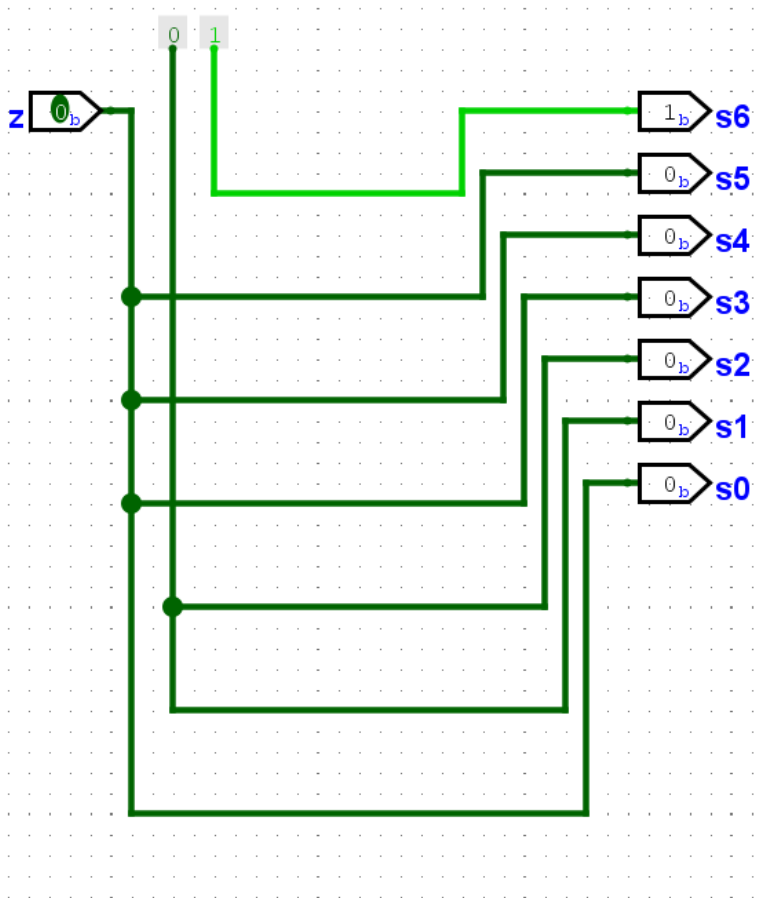

Comparator

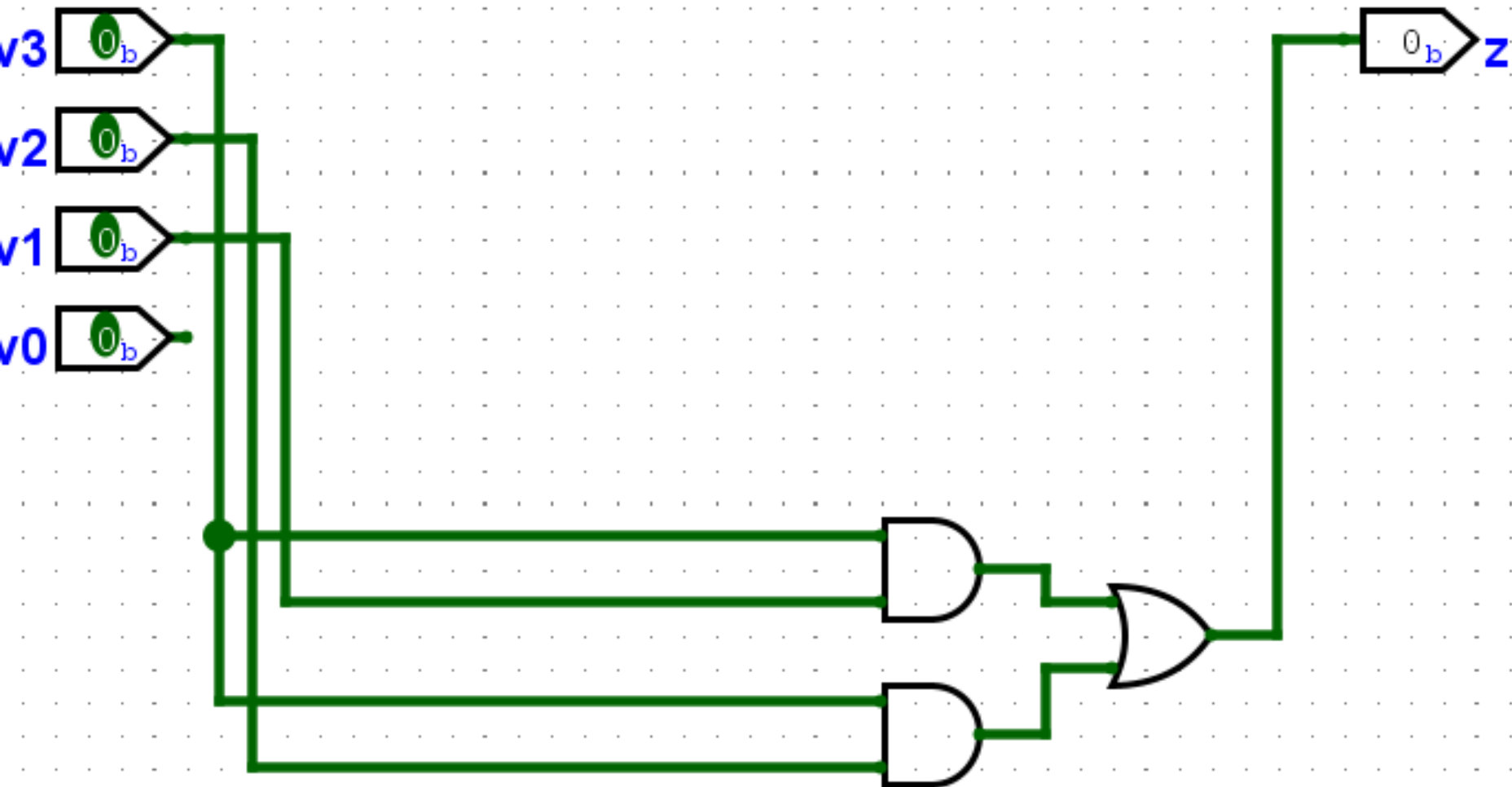

v_3	v_2	v_1	v_0	z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Working circuit

