

Lab 6

Marshall H

This counted down from 15.

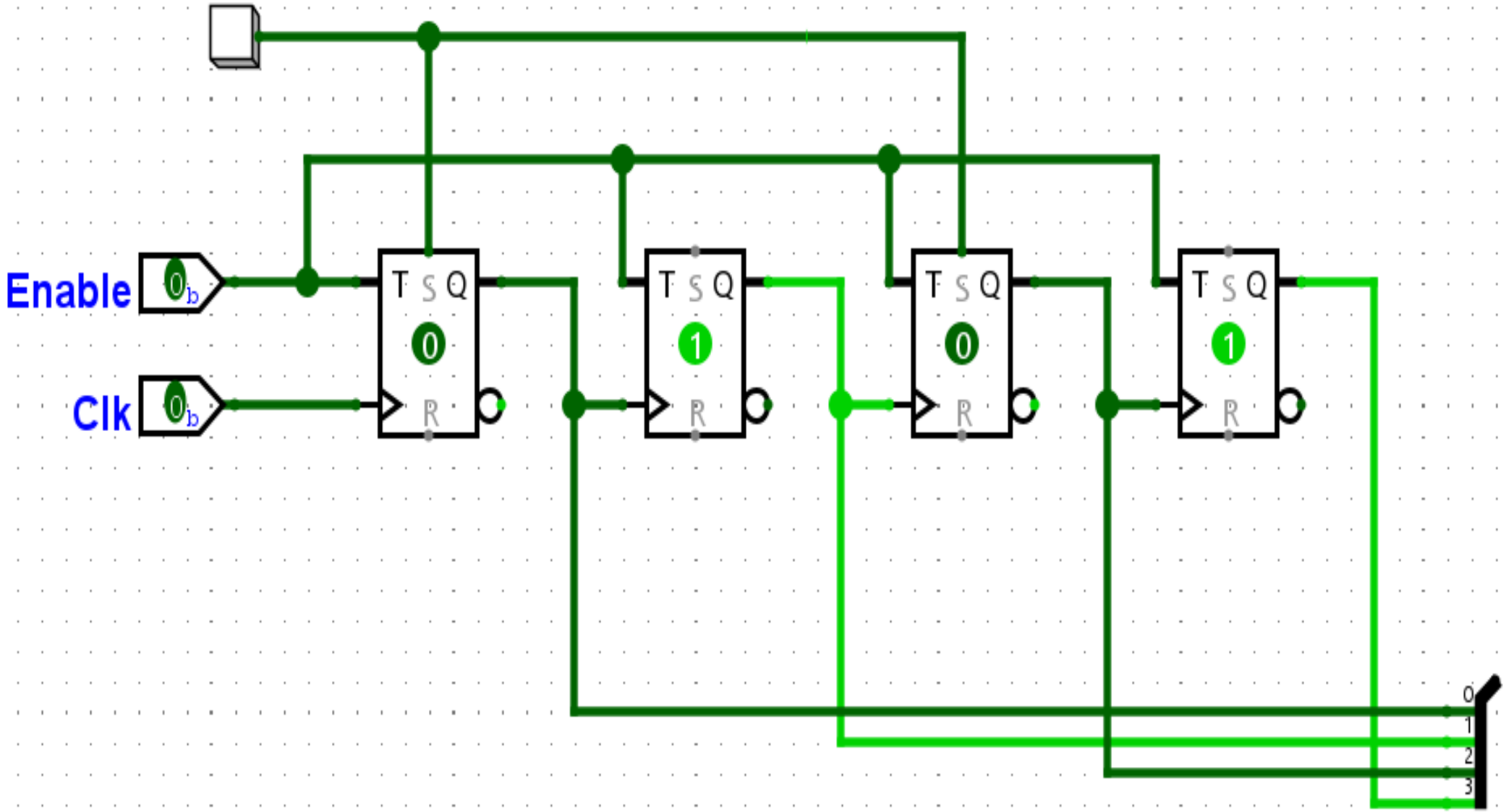


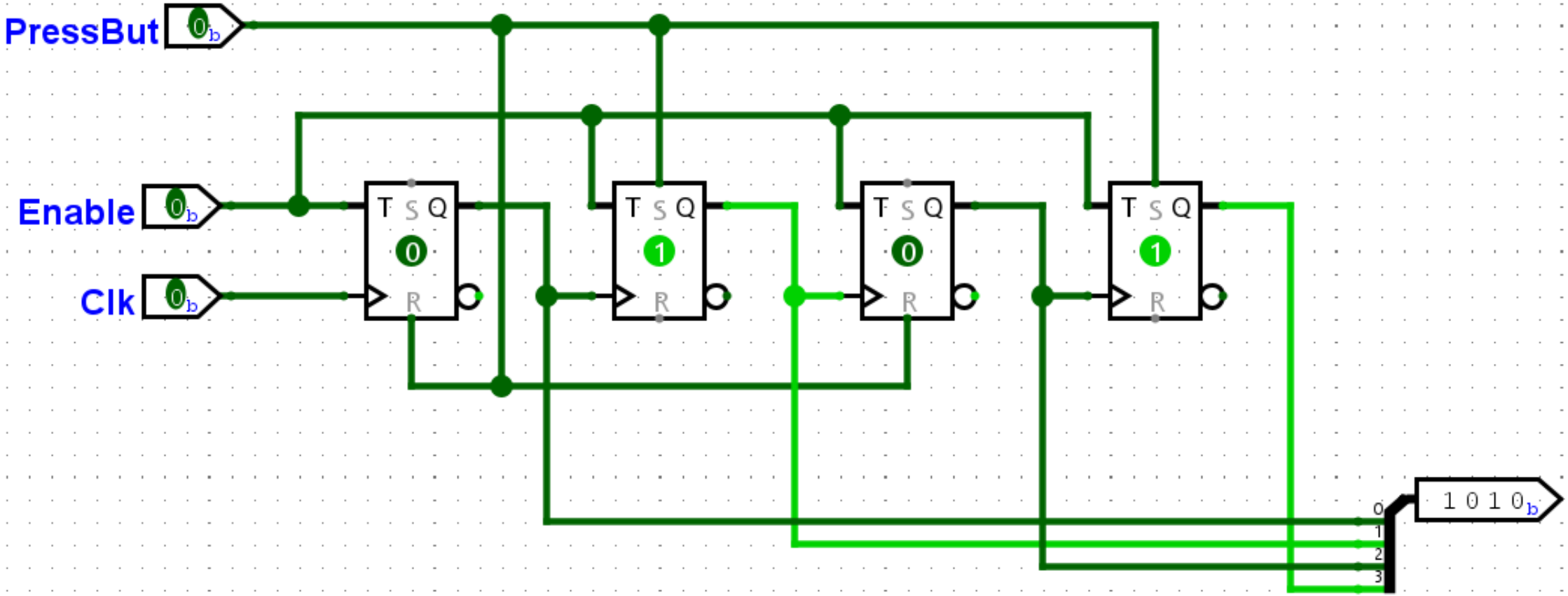Switch which flip flops the button goes into Sum. Was on 0 and 2, now on 1 and 3.




Have the button reset bits 0 and 2 to make it start at 1010, or 10 in decimal

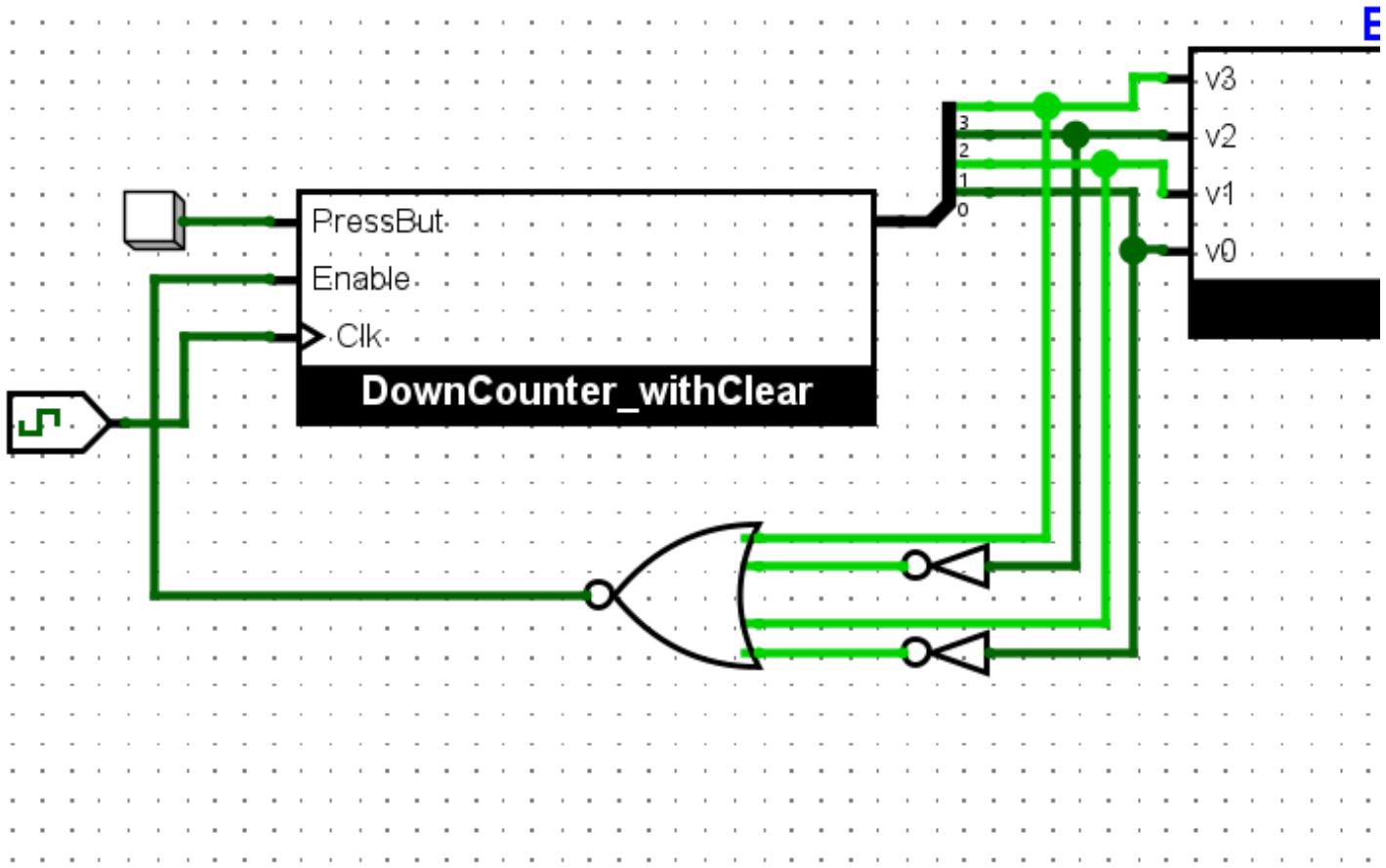The problem is that it does not stop after it gets to 0. It starts at 15 and goes down from there



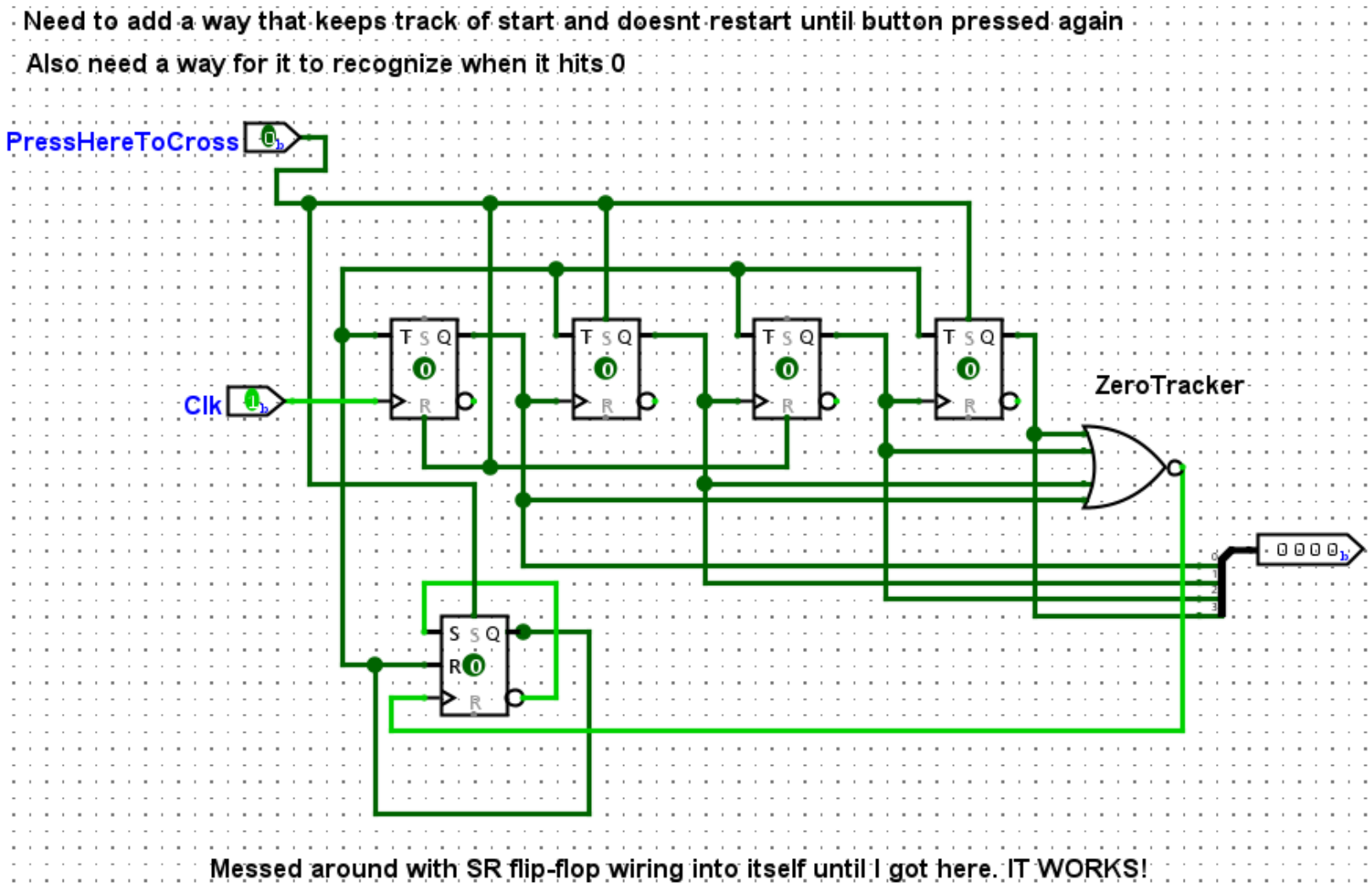- Trie to see what would happen here. Did not work clearly but I will mess around with this more



- Put the NOR gate in the circuit.
- Messed round with different gates but ultimately figured SR would be best for the memory application of holding ON until the counter hits 0000
- Video in GitHub