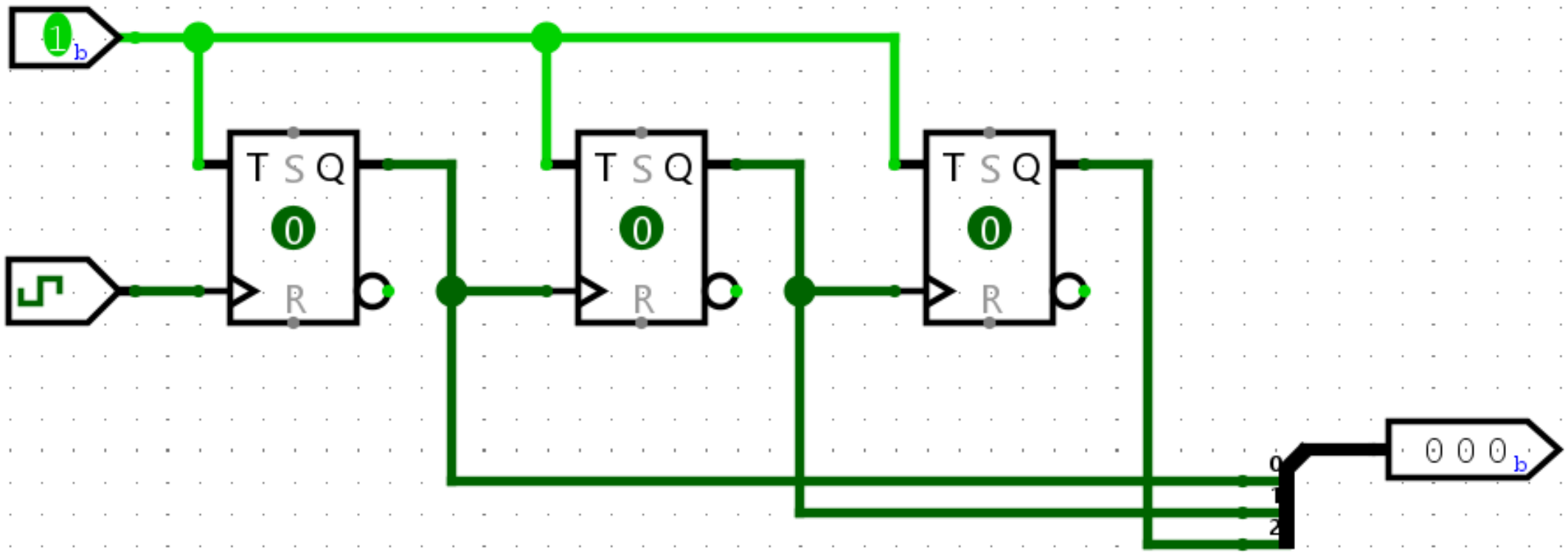
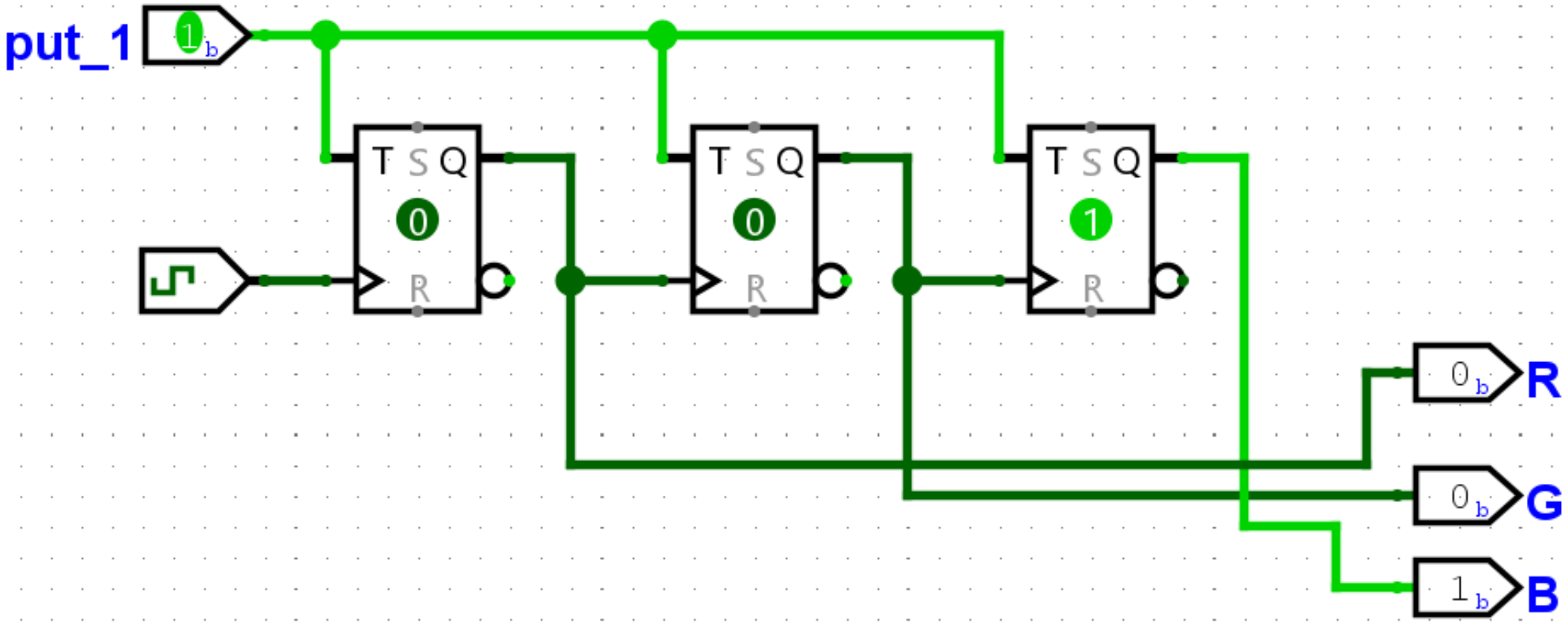
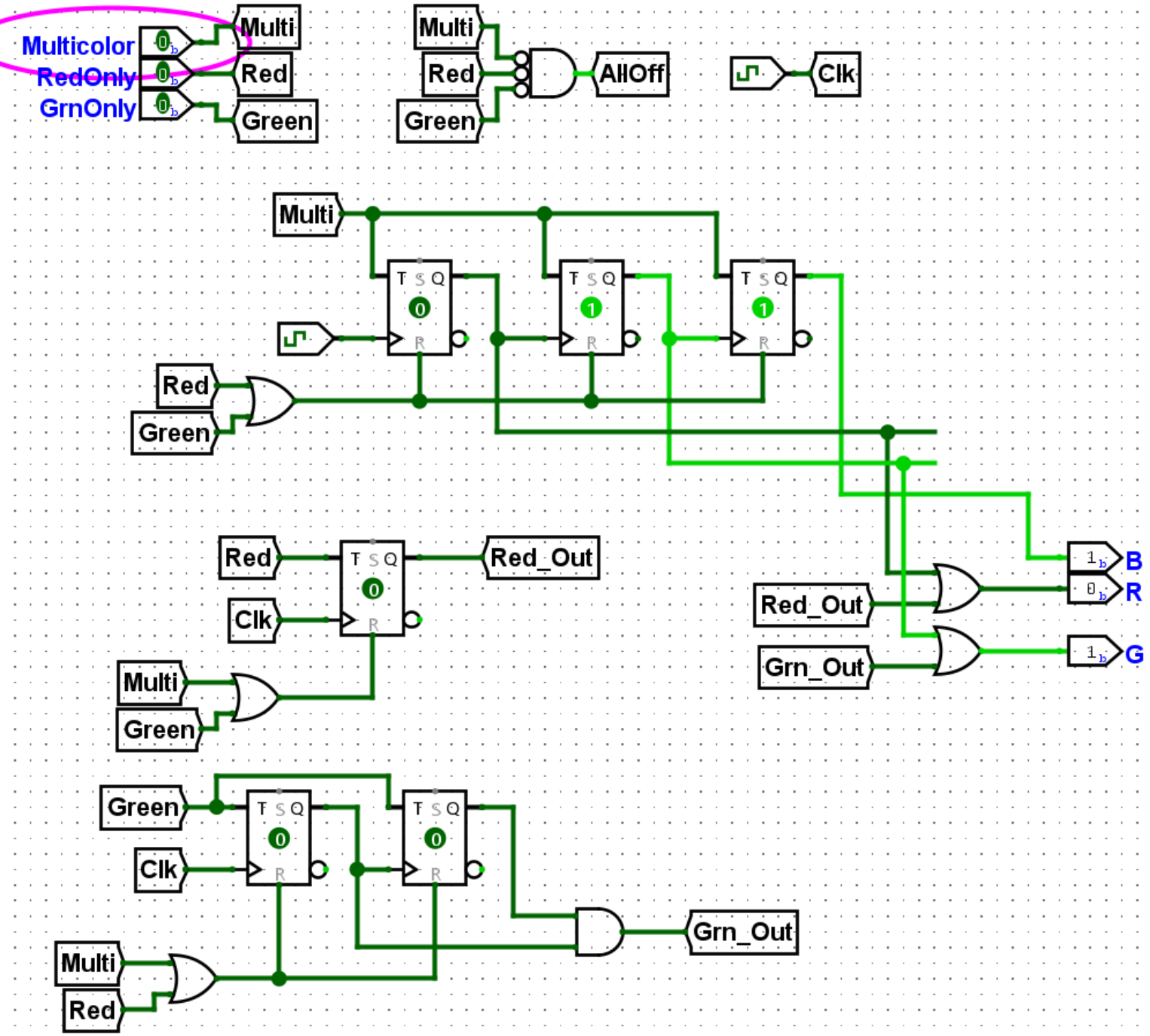

1
b
T S Q
0
R
T S Q
0
R
T S Q
0
R
0 0 0
b



- Split outputs into 3 separate bits. Shows 8 different color modes



- Final design for 3 different light states.
- Down counter for 8-different color state
- Turns light off if more than 1 switch is enabled
- Added flip flop on green so that the blinking rate is different